

# ASSEMBLY ASSIGNMENT

R.Radhika  
r170234@rguktrkv.ac.in  
IITH - Future Wireless Communications (FWC)

19-09-2022

## Contents

## 3 PIN Diagram

## Abstract

This manual shows that move the content of one register to another register :

## 1 Introduction

### 1.1 7474 IC:

This IC contains 2 D-flip flops.  
For this section total of 4 flip-flops(2 ICs) are required since we need to design a 4-bit shift register.

### 1.2 Arduino:

In Arduino Uno we generate the clock pulse which is given to the each and every flip-flop by default.  
We take 5 volts and Ground as the supply to the bread board from the Arduino board.

## 2 Components

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	20
Breadboard		1
IC	7447	2

# 7474

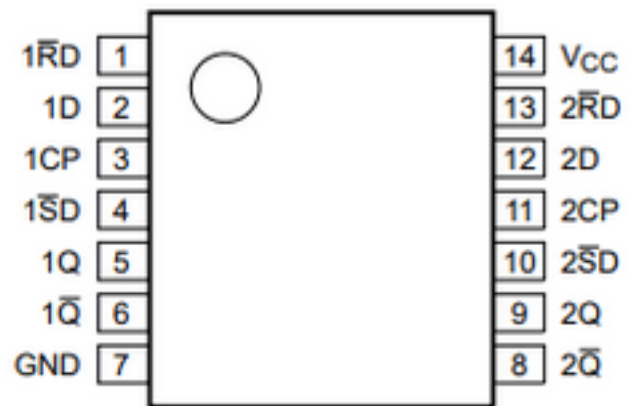


Figure.a

## 4 Truth Table


D1	Q1=D2	Q2=D3	Q3=D4	Q4
0	0	0	0	0
1	1	0	0	0
1	1	1	0	0
0	0	1	1	0
0	0	0	1	1
0	0	0	0	1
0	0	0	0	0

Truth table for 0110

## 5 Circuit Diagram

Figure.b

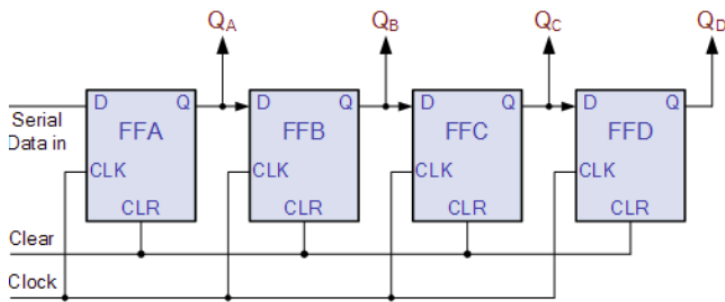**4-bit shift register:** 1.It has 4 D-flip flops.  
2.Verify the output for the sequence by changing the D1 pin to Vcc and Ground for different clock cycles.  
3.It has 4 outputs i.e Q1, Q2, Q3 and Q4.



4. We need to give the input from MSB to LSB.

## 6 Implementation

### Connections

**Problem-1** 1. Connect the circuit as per the above diagram.

2. Execute the circuit using the below code.

<https://github.com/Radhikarkv/fwcproject.git>

**Problem-2** 1. Same circuit can be implemented by without IC display to the Q1, Q2, Q3 AND Q4 respectively.

2. Execute the circuit using the below code.

<https://github.com/Radhikarkv/fwcproject.git>