

# ARM ASSIGNMENT

R.Radhika  
r170234@rguktrkv.ac.in  
IITH - Future Wireless Communications (FWC)

19-09-2022

## Contents

<b>1 Introduction</b>	<b>1</b>
1.1 7474 IC: . . . . .	1
1.2 Arduino: . . . . .	1
<b>2 Components</b>	<b>1</b>
<b>3 PIN Diagram</b>	<b>1</b>
<b>4 Truth Table</b>	<b>1</b>
<b>5 Circuit Diagram</b>	<b>1</b>
<b>6 Implementation</b>	<b>2</b>
<b>7 Setup</b>	<b>2</b>
7.1 The steps for implementation: . . . . .	2

## 3 PIN Diagram

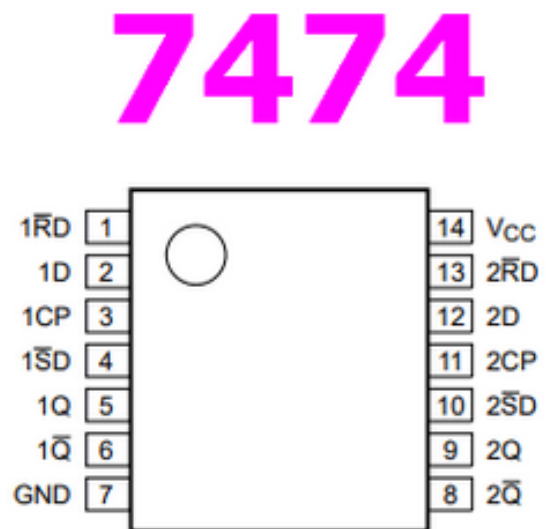


Figure.a

## Abstract

This manual shows that move the content of one register to another register :

## 4 Truth Table

D1	Q1=D2	Q2=D3	Q3=D4	Q4
0	0	0	0	0
1	1	0	0	0
1	1	1	0	0
0	0	1	1	0
0	0	0	1	1
0	0	0	0	1
0	0	0	0	0

Truth table for 0110

## 1 Introduction

### 1.1 7474 IC:

This IC contains 2 D-flip flops.  
For this section total of 4 flip-flops(2 ICs) are required since we need to design a 4-bit shift register.

### 1.2 Arduino:

In Arduino Uno we generate the clock pulse which is given to the each and every flip-flop by default.  
We take 5 volts and Ground as the supply to the bread board from the Arduino board.


## 5 Circuit Diagram

Figure.b

## 2 Components

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	20
Breadboard		1
IC	7447	2

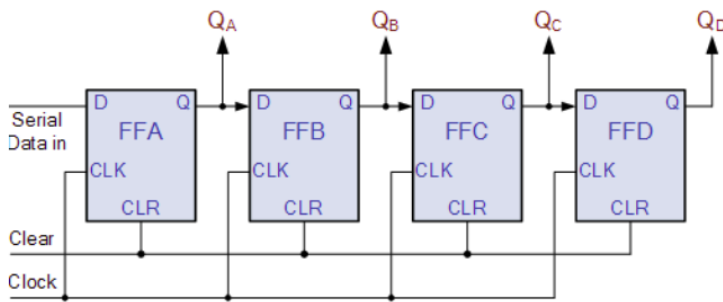- 4-bit shift register:**
- 1.It has 4 D-flip flops.
  - 2.Verify the output for the sequence by changing the D1 pin to Vcc and Ground for different clock cycles.
  - 3.It has 4 outputs i.e Q1, Q2, Q3 and Q4.
  4. We need to give the input from MSB to LSB.



```
scp /data/data/com.termux/files/home/arm/codes/
GCC.Project/output/bin/codes.bin
usernameofpc@IPaddress:/home/username
```

Make sure that the appropriate username, IP address of the Laptop is given in the above command.

2. Now execute the following commands on the Laptop terminal

Make sure that required installation of programmer application and modification of bash file had done prior executing below command

```
bash flash.sh codes.bin
```

## 6 Implementation

Ard	D13	D13				Vcc	Vcc	Vcc	Vcc	Vcc	Gnd				
7474	3	11	5-12	9		1	4	10	13	14	7	5	9		
7474	3	11		2	5-12	1	4	10	13	14	7			5	9
LED												led1	led2	led3	led4

Connections

- Problem-1**
1. Connect the circuit as per the above diagram.
  2. Execute the circuit using the below code.

- Problem-2**
1. Same circuit can be implemented by without IC display to the Q1, Q2, Q3 AND Q4 respectively.
  2. Execute the circuit using the below code.

```
https://github.com/Radhikarkv/fwcproject.git
```

## 7 Setup

1. Connect the Vaman to the Laptop through USB.
2. There is a button and an LED to the left of the USB port on the Vaman. There is another button to the right of the LED.
3. Press the right button first and immediately press the left button. The LED will be blinking green. The Vaman is now in bootloader mode.

### 7.1 The steps for implementation:

1. Login to termux-ubuntu on the android device and execute the following commands:  
Make sure that the required installation of pygmy-sdk had done prior executing below commands

```
proot--distro login debian
cd /data/data/com.termux/files/home/
mkdir arm
svn co https://github.com/Radhikarkv/fwcproject.git
```

```
cd codes/GCC_Project
make
```